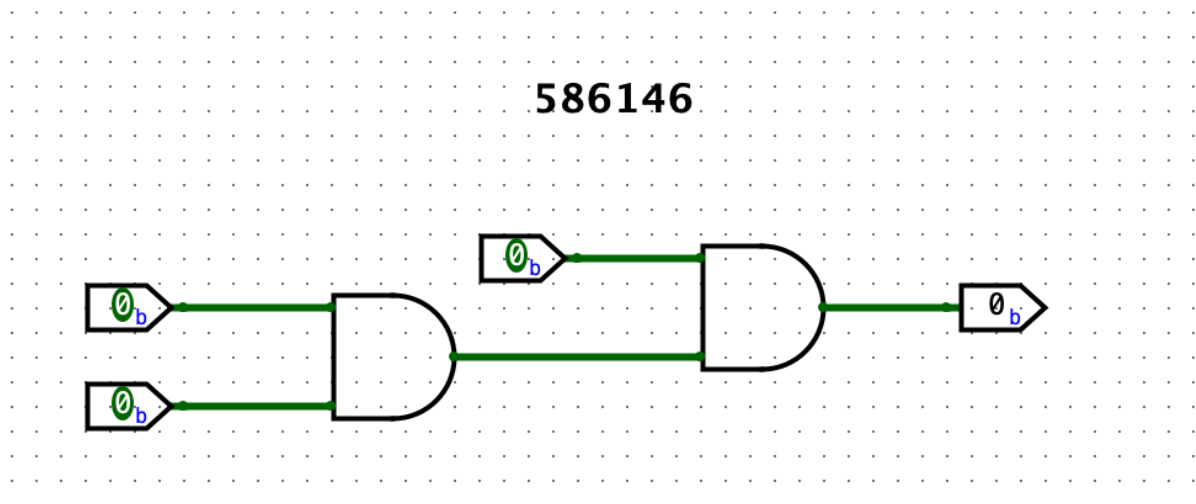


Template Week 2 – Logic

Student number: 586146

Assignment 2.1: Parking lot

We need AND gates (two of them).




Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Assignment 2.2: Android or iPhone

We need a XOR gate.

586146

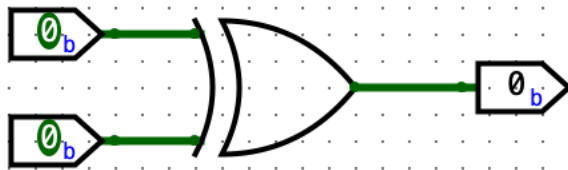

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
0	1	1
1	0	1
1	1	0

Assignment 2.3: Four NAND gates

Complete this table


A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

We could simplify this gate by making use of a XOR gate.


Assignment 2.4: Getting to know Logisim evolution

Screenshot of the design with your name and student number in it:

586146

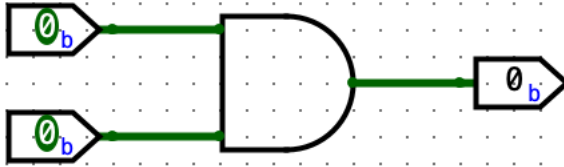


586146

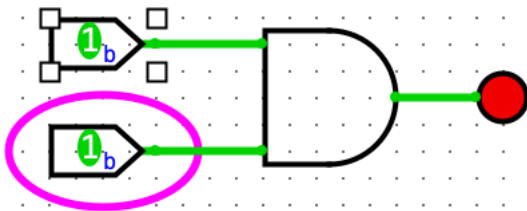

Assignment 2.5: SR Latch


Screenshot SR Latch in Logisim with your name and student number:

586146

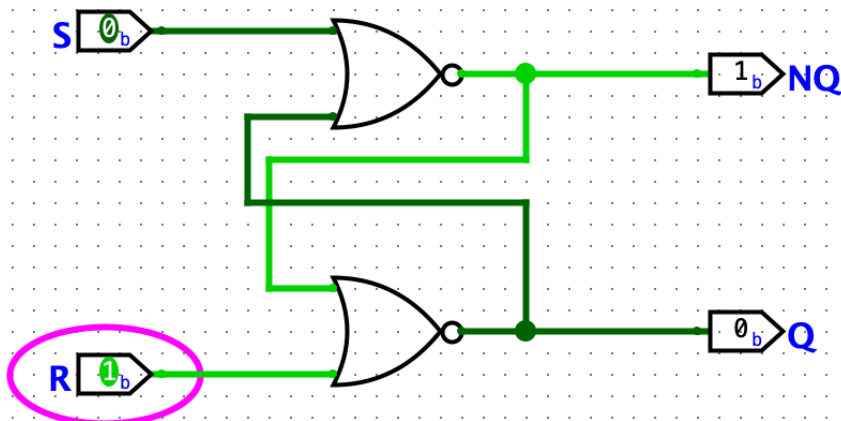

Assignment 2.6: Vending Machine

Screenshot Vending Machine in Logisim with your name and student number:

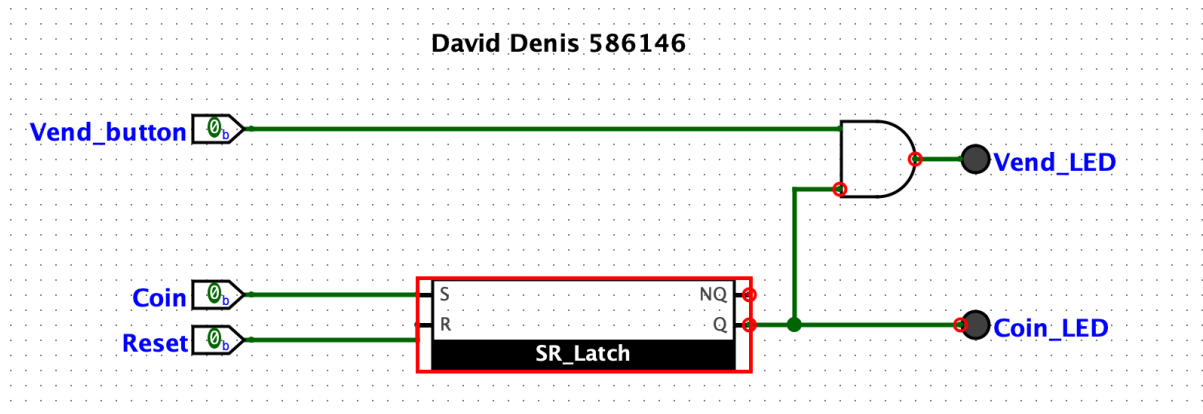

Assignment 2.7: Bitwise operators

Complete the java source code for bitwise operators. Put the source code here.

Even or Odd:

```
public class Main {  
    public static void main(String[] args) {  
        int number = 5;  
  
        if ((number & 1) == 1)  
            System.out.println("number is odd");  
        else  
            System.out.println("number is even");  
    }  
}
```

Power of 2:

```
public class Main {  
    public static void main(String[] args) {  
        int number = 4;  
  
        if ((number & (number - 1)) == 0 && number > 0)  
            System.out.println("number is a power of 2");  
        else  
            System.out.println("number isn't a power of 2");  
    }  
}
```

Assignment 2.8: Java Application Bit Calculations

Create a java program that accepts user input and presents a menu with options.


1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Keep this application because you need to expand it in week 6 for calculating network segments.

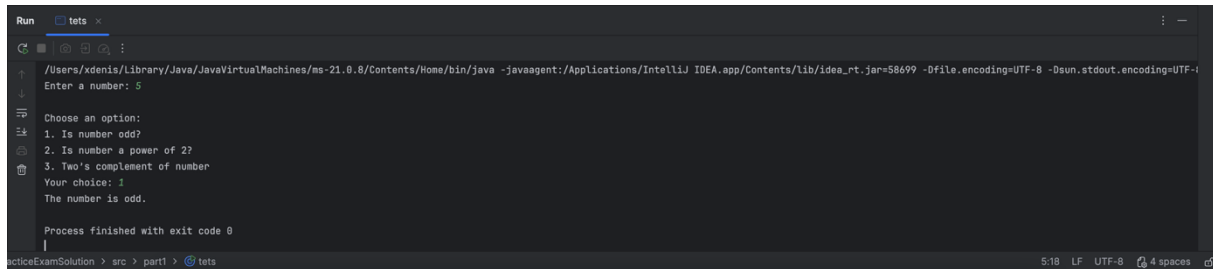Paste source code here, with a screenshot of a working application.



```
Run tests x
/Users/xdenis/Library/Java/JavaVirtualMachines/ms-21.0.8/Contents/Home/bin/java -javaagent:/Applications/IntelliJ IDEA.app/Contents/lib/idea_rt.jar=58699 -Dfile.encoding=UTF-8 -Dsun.stdout.encoding=UTF-8
Enter a number: 5
Choose an option:
1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number
Your choice: 1
The number is odd.
Process finished with exit code 0
```

```
package part1;
```

```
import java.util.Scanner;
```

```
public class tets {
```

```
    // Even or Odd
```

```
    public static boolean isOdd(int n) {
```

```
        return (n & 1) == 1;
```

```
    }
```

```
    // Power of 2
```

```
    public static boolean isPowerOfTwo(int n) {
```

```
        return n > 0 && (n & (n - 1)) == 0;
```

```
    }
```

```
    // 3. Two's complement
```

```
    public static int twosComplement(int n) {
```

```
        return (~n) + 1;
```

```
    }
```

```

public static void main(String[] args) {

    Scanner scanner = new Scanner(System.in);

    System.out.print("Enter a number: ");
    int number = scanner.nextInt();

    System.out.println("\nChoose an option:");
    System.out.println("1. Is number odd?");
    System.out.println("2. Is number a power of 2?");
    System.out.println("3. Two's complement of number");

    System.out.print("Your choice: ");
    int choice = scanner.nextInt();

    switch (choice) {
        case 1:
            if (isOdd(number))
                System.out.println("number is odd.");
            else
                System.out.println("number is even.");
            break;

        case 2:
            if (isPowerOfTwo(number))
                System.out.println("number is a power of 2.");
            else
                System.out.println("number isn't a power of 2.");
            break;

        case 3:
            System.out.println("Two's complement: " + twosComplement(number));
    }
}

```

```
        break;

    default:
        System.out.println("Invalid option.");
    }

    scanner.close();
}
```

Ready? Then save this file and export it as a pdf file with the name: [week2.pdf](#)